

Key
Example 1.1 : A silicon diode has a reverse saturation current of 7.12 nA at room temperature of 27 °C. Calculate its forward current if it is forward biased with a voltage of 0.7 V.

Solution : The given values are, $I_0 = 7.12 \text{ nA} = 7.12 \times 10^{-9} \text{ A}$, $V = + 0.7 \text{ V}$ as forward biased.

$\eta = 2$ for silicon diode,

$$T = 27^\circ\text{C} = 27 + 273 = 300^\circ\text{K}$$

$$\text{Now } V_T = kT = 8.62 \times 10^{-5} \times 300 = 0.026 \text{ V}$$

According to diode current equation,

$$I = I_0 (e^{V/\eta V_T} - 1)$$

$$\begin{aligned} \therefore I &= 7.12 \times 10^{-9} (e^{0.7/2 \times 0.026} - 1) \\ &= 7.12 \times 10^{-9} [701894.59 - 1] = 4.99 \times 10^{-3} \text{ A} \approx 5 \text{ mA} \end{aligned}$$

Thus the forward current is 5 mA

Example 1.2 : The voltage across a silicon diode at room temperature of 300 °K is 0.71 V when 2.5 mA current flows through it. If the voltage increases to 0.8 V, calculate the new diode current.

Solution : The current equation of a diode is

$$I = I_0 (e^{V/\eta V_T} - 1)$$

$$\text{At } 300^\circ\text{K, } V_T = 26 \text{ mV} = 26 \times 10^{-3} \text{ V}$$

$$V = 0.71 \text{ V for } I = 2.5 \text{ mA and } \eta = 2 \text{ for silicon}$$

$$\therefore 2.5 \times 10^{-3} = I_0 [e^{(0.71/2 \times 26 \times 10^{-3})} - 1]$$

$$\therefore I_0 = 2.93 \times 10^{-9} \text{ A}$$

$$\text{Now } V = 0.8 \text{ V}$$

$$\therefore I = 2.93 \times 10^{-9} [e^{(0.8/2 \times 26 \times 10^{-3})} - 1]$$

$$= 0.0141 \text{ A} = 14.11 \text{ mA}$$

►►► **Example 2.1 :** A half wave rectifier circuit is supplied from a 230 V, 50 Hz supply with a step down ratio of 3:1 to a resistive load of 10 k Ω . The diode forward resistance is 75 Ω while transformer secondary resistance is 10 Ω . Calculate maximum, average, RMS values of current, D.C. output voltage, efficiency of rectification and ripple factor.

Solution : The circuit is shown in the Fig. 2.8.

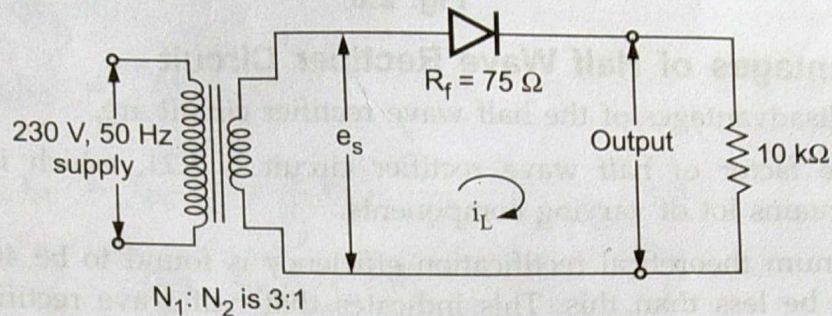


Fig. 2.8

The given values are,

$$R_f = 75 \Omega, R_L = 10 \text{ k}\Omega, R_s = 10 \Omega.$$

The given supply voltages are always r.m.s. values.

$$E_p(\text{R.M.S.}) = 230 \text{ V}, \quad \frac{N_1}{N_2} = \frac{3}{1} \text{ i.e. } \frac{N_2}{N_1} = \frac{1}{3}$$

$$\frac{N_2}{N_1} = \frac{E_s(\text{R.M.S.})}{E_p(\text{R.M.S.})}$$

$$\therefore \frac{1}{3} = \frac{E_s(\text{R.M.S.})}{230}$$

$$\therefore E_s(\text{R.M.S.}) = 76.667 \text{ V}$$

This is r.m.s. value of the transformer secondary voltage.

$$\therefore E_{sm} = \sqrt{2} E_s(\text{R.M.S.}) = \sqrt{2} \times 76.667 = 108.423 \text{ V}$$

$$\begin{aligned} \therefore I_m &= \frac{E_{sm}}{R_s + R_f + R_L} = \frac{108.423}{10 + 75 + 10 \times 10^3} \\ &= 10.75 \text{ mA} \end{aligned}$$

$$\therefore I_{av} = I_{DC} = \frac{I_m}{\pi} = \frac{10.75}{\pi} = 3.422 \text{ mA}$$

$$I_{RMS} = \frac{I_m}{2} \text{ for half wave}$$

$$= \frac{10.75}{2} = 5.375 \text{ mA}$$

$$E_{DC} = \text{d.c output voltage} = I_{DC} R_L$$

$$= 3.422 \times 10^{-3} \times 10 \times 10^3 = 34.22 \text{ V}$$

$$P_{DC} = \text{d.c. output power} = E_{DC} I_{DC} = 34.22 \times 3.422 \times 10^{-3}$$

$$= 0.1171 \text{ W}$$

This also can be obtained as,

$$P_{DC} = \frac{I_m^2}{\pi^2} R_L = \frac{(10.75 \times 10^{-3})^2}{\pi^2} \times 10 \times 10^3$$

$$= 0.1171 \text{ W}$$

$$P_{AC} = \text{a.c. input power} = I_{RMS}^2 [R_s + R_f + R_L]$$

$$= (5.375 \times 10^{-3})^2 [10 + 75 + 10 \times 10^3] = 0.2913 \text{ W}$$

$$\therefore \% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.1171}{0.2913} \times 100 = 40.19 \%$$

The ripple factor is constant for half wave rectifier and is 1.21.

$$\therefore \gamma \equiv 1.21$$

►►► **Example 2.3 :** A voltage $V = 300 \cos 100 t$ is applied to a half wave rectifier, with $R_L = 5 \text{ k}\Omega$. The rectifier may be represented by ideal diode in series with a resistance of $1 \text{ k}\Omega$. Calculate

- i) I_m ii) D.C. power iii) A.C. power iv) Rectifier efficiency and v) Ripple factor.

Solution : The diode circuit is as shown in the Fig. 2.10.

The given voltage is $V = 300 \cos 100 t$ volts

Compare with, $E = E_{sm} \sin \omega t$

$$E_{sm} = 300 \text{ volts}$$

$R = 1 \text{ k}\Omega$ = Resistance in series with diode

$$R_L = 5 \text{ k}\Omega, R_s = R_f = 0 \Omega$$

$$\text{i) } I_m = \frac{E_{sm}}{R + R_L + R_f + R_s} = \frac{300}{6 \times 10^3} = 50 \text{ mA.}$$

$$\text{ii) } I_{DC} = \frac{I_m}{\pi} = \frac{50}{\pi} = 15.9154 \text{ mA}$$

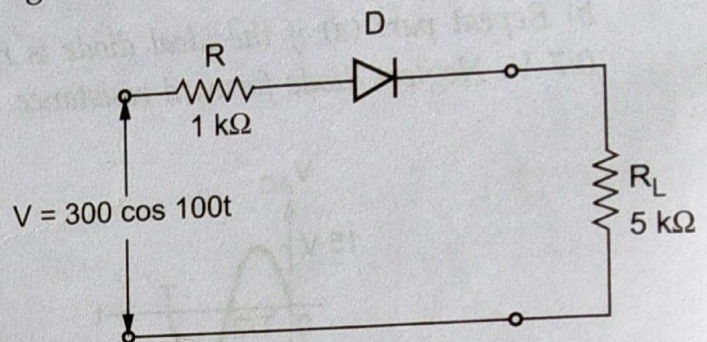


Fig. 2.10

$$\therefore P_{DC} = I_{DC}^2 R_L = (15.9154 \times 10^{-3})^2 \times 5 \times 10^3$$

$$= 1.2665 \text{ watts}$$

$$\text{iii) } P_{AC} = I_{RMS}^2 (R + R_L + R_s + R_f)$$

$$= \left(\frac{I_m}{2} \right)^2 (R + R_L + R_s + R_f) \text{ as } I_{RMS} = \frac{I_m}{2} \text{ for half wave}$$

$$= \left(\frac{50 \times 10^{-3}}{2} \right)^2 \times 6 \times 10^3 = 3.75 \text{ watts}$$

$$\text{iv) } \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{1.2665}{3.75} \times 100$$

$$= 33.77 \%$$

$$\text{v) } \text{Ripple factor} = \sqrt{\left(\frac{I_{RMS}}{I_{DC}} \right)^2 - 1} = \sqrt{\left(\frac{25 \times 10^{-3}}{15.9154 \times 10^{-3}} \right)^2 - 1}$$

$$= 1.211$$

►►► **Example 2.4 :** A half wave rectifier circuit connected to a 230 V, 50 Hz source, through a transformer of turn ratio of 10 : 1. The rectifier circuit is to supply power to a 500 Ω , 1 watt resistor and diode forward resistance is 100 Ω .

Calculate :

- 1) Maximum, average and r.m.s. value of current and voltage.
- 2) Efficiency of rectification.
- 3) Percentage regulation.

Solution : $E_{p(r.m.s.)} = 230 \text{ V}$, $N_1/N_2 = 10:1$, $R_L = 500 \Omega$, $R_f = 100 \Omega$

$$\frac{N_2}{N_1} = \frac{1}{10} = \frac{E_{s(r.m.s.)}}{E_{p(r.m.s.)}}$$

$$\therefore E_{s(r.m.s.)} = \frac{1}{10} \times 230 = 23 \text{ V}$$

$$\therefore E_{sm} = \sqrt{2} \times E_{s(r.m.s.)} = \sqrt{2} \times 23 = 32.5269 \text{ V.}$$

$$\text{1) } \therefore I_m = \frac{E_{sm}}{R_f + R_L} = \frac{32.5269}{100 + 500} = 54.2115 \text{ mA} \quad \dots \text{Maximum current}$$

$$\therefore I_{av} = I_{DC} = \frac{I_m}{\pi} = 17.2561 \text{ mA} \quad \dots \text{Average current}$$

$$\therefore I_{R.M.S.} = \frac{I_m}{2} \text{ for half wave} = 27.1058 \text{ mA}$$

$$\therefore E_{DC} = I_{DC} R_L = 8.628 \text{ V}$$

$$2) \therefore P_{DC} = I_{DC}^2 R_L = 0.14888 \text{ W}$$

$$P_{AC} = I_{RMS}^2 (R_L + R_f) = 0.44083 \text{ W}$$

$$\therefore \% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.14888}{0.44083} \times 100 = 33.7723 \%$$

$$3) (V_{d.c.})_{NL} = \frac{E_{sm}}{\pi} = \frac{32.5269}{\pi} = 10.3536 \text{ V}$$

$$(V_{d.c.})_L = E_{DC} = 8.628 \text{ V}$$

$$\therefore \% R = \frac{(V_{dc})_{NL} - (V_{dc})_L}{(V_{dc})_L} \times 100 = 20 \%$$

►►► **Example 2.5 :** In a centre-tapped full wave rectifier, the rms half secondary voltage is 9 V. Assuming ideal diodes and load resistance $R_L = 1 \text{ k}\Omega$, find :

i) Peak current ii) D.C. load voltage iii) R.M.S. current iv) Ripple factor v) Efficiency.

Solution : $E_s(\text{r.m.s.}) = 9 \text{ V}$, $R_L = 1 \text{ k}\Omega$

$$\text{i)} \quad I_m = \frac{E_{sm}}{R_L}$$

$$\text{Now} \quad E_{sm} = \sqrt{2}E_s(\text{r.m.s.}) = \sqrt{2} \times 9 = 12.7279 \text{ V}$$

$$\therefore \quad I_m = \frac{12.7279}{1 \times 10^3} = 12.7279 \text{ mA} \quad \dots \text{Peak current}$$

$$\text{ii)} \quad I_{DC} = \frac{2I_m}{\pi} = \frac{2 \times 12.7279}{\pi} = 8.1028 \text{ mA}$$

$$\therefore \quad E_{DC} = I_{DC}R_L = 8.1028 \times 10^{-3} \times 1 \times 10^3 = 8.1028 \text{ V}$$

$$\text{iii)} \quad I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{12.7279}{\sqrt{2}} = 9 \text{ mA}$$

$$\begin{aligned} \text{iv)} \quad \text{Ripple factor} &= \sqrt{\left[\frac{I_{RMS}}{I_{DC}}\right]^2 - 1} = \sqrt{\left(\frac{9}{8.1028}\right)^2 - 1} \\ &= 0.48 \end{aligned}$$

$$\text{v)} \quad P_{DC} = I_{DC}^2 R_L = (8.1028)^2 \times 1 \times 10^3 = 65.65 \text{ mW}$$

$$P_{AC} = I_{RMS}^2 R_L = (9)^2 \times 1 \times 10^3 = 81 \text{ mW}$$

$$\therefore \quad \% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{65.65}{81} \times 100 = 81.04 \%$$

» **Example 2.9 :** The four semiconductor diodes used in a bridge rectifier circuit each having a forward resistance of 0.1Ω and infinite reverse resistance, feed a d.c. current of 10 A to a resistive load from a sinusoidally varying alternating supply of 30 V (r.m.s). Determine the resistance of the load and the efficiency of the circuit.

Solution : The given values are,

$$R_f = 0.1 \Omega, I_{DC} = 10 \text{ A}, R_s = 0 \Omega, E_s(\text{R.M.S.}) = 30 \text{ V}$$

Now
$$E_{sm} = E_{sm}(\text{R.M.S.}) \times \sqrt{2} = \sqrt{2} \times 30$$

$$= 42.4264 \text{ V}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

\therefore
$$I_m = \frac{\pi \times I_{DC}}{2} = \frac{\pi \times 10}{2} = 15.7079 \text{ A}$$

$$\text{Now} \quad I_m = \frac{E_{sm}}{2R_f + R_s + R_L}$$

$$\therefore 15.7079 = \frac{42.4264}{2 \times 0.1 + R_L}$$

$$\therefore R_L + 0.2 = 2.7$$

$$\therefore R_L = 2.5 \, \Omega$$

$$\text{Now} \quad P_{DC} = I_{DC}^2 R_L = (10^2) \times 25 = 250 \, \text{W}$$

$$P_{AC} = I_{RMS}^2 (2R_f + R_s + R_L)$$

$$\text{and} \quad I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{15.7079}{\sqrt{2}} = 11.1071 \, \text{A}$$

$$\therefore P_{AC} = (11.1071)^2 [2 \times 0.1 + 2.5] = 333.092 \, \text{W}$$

$$\therefore \% \eta = \frac{P_{DC}}{P_{AC}} \times 100$$

$$= \frac{250}{333.092} \times 100$$

$$= 75.05 \% \quad \dots \text{Rectifier efficiency}$$

$$= 0.28 \text{ V}$$

» **Example 2.39 :** A 230 V, 60 Hz voltage is applied to the primary of a 5 : 1 step down, center tapped transformer used in the full wave rectifier having a load of 900Ω . If the diode resistance and the secondary coil resistance together has a resistance of 100Ω , determine :

- i) d.c. voltage across the load
- ii) d.c. current flowing through the load
- iii) d.c. power delivered to the load
- iv) PIV across each diode
- v) ripple voltage and its frequency.

JNTU : May-2003, Set-1 ; May - 2004, Set-4; June-2009, Set-1, 2

Solution :

$$\frac{N_2}{N_1} = \frac{2E_{s(rms)}}{E_{p(rms)}}$$

$$\dots E_{p(rms)} = 230 \text{ V}$$

$$\therefore \frac{1}{5} = \frac{2 E_{s(rms)}}{230}$$

$$\therefore E_{s(rms)} = 23 \text{ V (each half)}$$

$$R_L = 900 \Omega$$

$$R_s + R_f = 100 \Omega$$

$$I_m = \frac{E_{sm}}{R_L + R_s + R_f}$$

$$= \frac{\sqrt{2} \times E_{s(rms)}}{R_L + R_s + R_f} = \frac{\sqrt{2} \times 23}{900 + 100} = 0.03252 \text{ A}$$

$$\therefore I_{DC} = \frac{2I_m}{\pi} = \frac{2 \times 0.03252}{\pi} = 0.0207 \text{ A}$$

$$\text{i) } E_{DC} = I_{DC} R_L = 0.0207 \times 900 = 18.6365 \text{ V}$$

$$\text{ii) } I_{DC} = 0.0207 \text{ A}$$

$$\text{iii) } P_{DC} = I_{DC}^2 R_L \text{ or } E_{DC} \times I_{DC} = 0.3857 \text{ W}$$

$$\text{iv) } PIV = 2 E_{sm} = 2 \times \sqrt{2} \times 23 = 65.0538 \text{ V}$$

$$\text{v) } \text{Ripple factor} = 0.482 = \frac{V_{r(rms)}}{E_{DC}}$$

$$\therefore \text{Ripple voltage} = V_{r(rms)} = 0.482 \times 18.6365 = 8.9827 \text{ V}$$

$$\text{Frequency of ripple} = 2f = 2 \times 60 = 120 \text{ Hz}$$

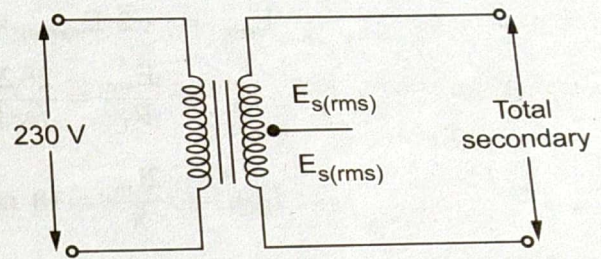


Fig. 2.66

➡ **Example 2.40 :** In a bridge rectifier the transformer is connected to 220 V, 60 Hz mains and the turns ratio of the step down transformer is 11 : 1. Assuming the diode to be ideal, find :

i) I_{DC} ii) voltage across the load iii) PIV.

Assume load resistance to be 1 k Ω .

JNTU : May-2003, Set-3

Solution : $\frac{N_2}{N_1} = \frac{1}{11}$, $E_{p(rms)} = 220$ V, $f = 60$ Hz, $R_L = 1$ k Ω

$$\frac{N_2}{N_1} = \frac{E_s(rms)}{E_p(rms)}$$

$$\therefore \frac{1}{11} = \frac{E_{s(rms)}}{220}$$

$$\therefore E_{s(rms)} = \frac{220}{11} = 20 \text{ V}$$

$$\therefore E_{sm} = \sqrt{2} E_{s(rms)} = 28.2842 \text{ V}$$

$$\text{i) } I_m = \frac{E_{sm}}{R_L} = \frac{28.2842}{1 \times 10^3} = 28.2842 \text{ mA}$$

$$\therefore I_{DC} = \frac{2I_m}{\pi} = 18 \text{ mA}$$

$$\text{ii) } E_{DC} = I_{DC} R_L = 18 \times 10^{-3} \times 1 \times 10^3 = 18 \text{ V}$$

$$\text{iii) } PIV = E_{sm} = 28.2842 \text{ V}$$

→ (or) Reverse breakdown

→ Peak Inverse voltage (PIV) (or) peak Reverse voltage (PRV) :

→ PIV refers to the maximum voltage a diode can withstand in the reverse-biased direction before breakdown.

→ PIV	→ Center-tapped FWR	→ $2V_m$
	→ Bridge Rectifier	→ V_m
	→ HWR	→ V_m