

→ ① % DC Current (δ) Average Current:

$$I_{dc} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \, d(\omega t) \quad \text{--- ①}$$

$$I_m = \frac{V_m}{(R_f + R_L)}$$

$$I_{dc} = \frac{1}{2\pi} \int_0^{\pi} \frac{I_m \sin \omega t \, d(\omega t)}{2\pi}$$

$$I_{dc} = \frac{I_m}{2\pi} \left[ -\cos \omega t \right]_0^{\pi}$$

$$I_{dc} = \frac{I_m}{2\pi} \left[ -(\cos \pi - \cos 0) \right] = \frac{I_m[-(-1-1)]}{2\pi}$$

$$I_{dc} = \frac{I_m}{2\pi}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{V_m}{\pi(R_f + R_L)}$$

--- ②

similarly

$$V_{dc} = \frac{V_m}{\pi} = \frac{I_m (R_f + R_L)}{\pi}$$

--- ③

→ (2) Voltage Regulation:

(2)

The variation of dc % voltage as a function of d.c. load current is called Regulation.

$$\% \text{ Regulation} = \frac{V_{\text{no load}} - V_{\text{full load}}}{V_{\text{full load}}} \times 100\%. \quad (2)$$

$$\% \text{ Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%. \quad (4)$$

$$V_{NL} = \frac{V_m}{\pi} \quad (5)$$

$$V_{FL} = \frac{V_m}{\pi} - I_{dc} R_f \quad (6)$$

$$V_{FL} = \frac{V_m}{\pi} - \frac{V_m}{\pi} \cdot \frac{R_f}{R_f + R_L}$$

$$V_{FL} = \frac{V_m}{\pi} \left[ 1 - \frac{R_f}{R_f + R_L} \right] = \frac{V_m}{\pi} \left[ \frac{R_f + R_L - R_f}{R_f + R_L} \right]$$

$$V_{FL} = \frac{V_m}{\pi} \left[ \frac{R_L}{R_f + R_L} \right] \quad (7)$$

Substitute eq (7) & eq (5) in eq (4).

$$\% \text{ Regulation} = \frac{\frac{V_m}{\pi} - \frac{V_m}{\pi} \left[ \frac{R_L}{R_f + R_L} \right]}{\frac{V_m}{\pi} \left[ \frac{R_L}{R_f + R_L} \right]}$$

$$\begin{aligned} \text{% Regulation} &= \frac{\frac{V_m}{\pi} \left[ 1 - \frac{R_L}{R_f + R_L} \right]}{\frac{V_m}{\pi} \left[ \frac{R_L}{R_f + R_L} \right]} \\ &= \frac{R_f + R_L - R_L}{R_f + R_L} \\ &\quad \frac{R_L}{R_f + R_L} \end{aligned}$$

$$\boxed{\text{% Regulation} = \frac{R_f}{R_L} \times 100}$$

(3) Root mean square current ( $I_{rms}$ ):

$$I_{rms} = \frac{1}{2\pi} \int_0^\pi I^2 d\theta \quad I = I_m \sin \theta$$

$$= \frac{1}{2\pi} \int_0^\pi I_m^2 \sin^2 \theta d\theta$$

$$= \frac{I_m^2}{2\pi} \int_0^\pi \left( \frac{1 - \cos 2\theta}{2} \right) d\theta$$

$$\therefore \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$= \frac{I_m^2}{4\pi} \left[ (\theta)_0^\pi - \left( \frac{\sin 2\theta}{2} \right)_0^\pi \right]$$

$$= \frac{I_m^2}{4\pi} \left[ (\pi - 0) - (0 - 0) \right] = \frac{I_m^2 \pi}{4\pi}$$

$$\therefore I_{rms} = \frac{I_m^2}{4} \quad \boxed{I_{rms} = \frac{I_m}{2}} \rightarrow (8)$$

④ Ripple factor:

(4)

$$r = \frac{\text{rms value of a.c. Components of o/p wave}}{\text{dc value of the o/p wave}}$$

$$r = \frac{I_{ac}}{I_{dc}} \quad \text{--- (9)}$$

The effective value of the pulsating o/p current

$$\begin{aligned} \tilde{I}_{rms} &= I_{ac} + \tilde{I}_{dc} \\ \sqrt{\tilde{I}_{rms}^2 - \tilde{I}_{dc}^2} &= I_{ae} \end{aligned}$$

$$r = \sqrt{\frac{\tilde{I}_{rms}^2 - \tilde{I}_{dc}^2}{\tilde{I}_{dc}^2}}$$

$$r = \sqrt{\left(\frac{\tilde{I}_{rms}}{\tilde{I}_{dc}}\right)^2 - \frac{\tilde{I}_{dc}^2}{\tilde{I}_{dc}^2}}$$

$$r = \sqrt{\left(\frac{\tilde{I}_{rms}}{\tilde{I}_{dc}}\right)^2 - 1} \quad \text{--- (10)}$$

or ② or ⑧ in ⑩

$$r = \sqrt{\left(\frac{\tilde{I}_{rms}/2}{\tilde{I}_{rms}/\pi}\right)^2 - 1}$$

$$r = \sqrt{\frac{\frac{\tilde{I}_{rms}}{2} \times \pi^2}{\tilde{I}_{rms}^2} - 1} = r = \sqrt{\frac{\pi^2}{4} - 1}$$

~~$r = 1.21$~~

⑤ Efficiency of Half wave Rectifiers :

⑤

$$\therefore \eta = \frac{P_{dc} \times 100}{P_{ac}} = \frac{\% \text{ DC power delivered to the Load}}{\text{i/p AC from the secondary winding}}$$

$$P_{dc} = I_{dc} R_L = \left( \frac{Im}{\pi} \right)^2 R_L \quad \text{--- (11)}$$

$$P_{dc} = \frac{Im^2}{\pi^2} R_L \quad \text{--- (12)}$$

$$P_{ac} = Im^2 (R_f + R_L)$$

$$= \frac{Im^2}{4} (R_f + R_L) \quad \text{--- (13)}$$

eq (12) & eq (13) in eq (11)

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{\frac{Im^2}{\pi^2} R_L}{\frac{Im^2}{4} (R_f + R_L)}$$

$$= \frac{\cancel{Im^2} R_L}{\cancel{\pi^2}} \times \frac{4}{\cancel{Im^2} (R_f + R_L)}$$

$$= \frac{4}{\pi^2} \frac{R_L}{R_f + R_L}$$

$$= \frac{4}{\pi^2} \frac{1}{\left( \frac{R_f}{R_L} + \frac{R_L}{R_f} \right)} = \frac{4}{\pi^2} \frac{1}{\left( 1 + \frac{R_f}{R_L} \right)}$$

If  $R_L \gg R_f$

$$\gamma = \frac{4}{\pi^2} = 0.406 \quad (6)$$

$\gamma \cdot \eta = 40.6\%$  ~~of the a.c. power is converted into d.c.~~

### ⑥ Transformer utilization factor (TUF):

$$TUF = \frac{\text{d.c. power delivered to the load}}{\text{a.c. power rating of the transformer secondary}} \quad (14)$$

$$TUF = \frac{P_{dc}}{P_{ac(\text{rated})}} \quad (15)$$

$$P_{ac(\text{rated})} = V_{ac(\text{rms})} \times I_{rms} \quad (16)$$

$$V_{ac(\text{rms})} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{2}$$

(17) (18)

$e_V(8)$  &  $e_V(7)$  in  $e_V(16)$

$$P_{ac(\text{rated})} = \frac{V_m}{\sqrt{2}} \frac{I_m}{2} \quad (18)$$

$$P_{dc} = I_{dc} R_L = \left(\frac{I_m}{\pi}\right)^2 R_L \quad (19)$$

$e_V(18)$  &  $e_V(19)$  in  $e_V(15)$ .

$$TUF = \frac{\left(\frac{Im}{\pi}\right)^2 RL}{\frac{Vm}{\sqrt{2}} \frac{Im}{2}}$$

$$Vm = Im (R_f + R_L)$$

$$\left[ Im = \frac{Vm}{R_f + R_L} \right]$$

$$TUF = \frac{\frac{Im^2 RL}{\pi^2}}{\frac{Im(R_f + R_L)}{\sqrt{2}} \frac{Im}{2}}$$

$$TUF = \frac{\frac{Im^2 RL}{\pi^2}}{\frac{Im^2 (R_f + R_L)}{2\sqrt{2}}} = \frac{Im^2 RL}{\pi^2} \times \frac{2\sqrt{2}}{Im^2 (R_f + R_L)}$$

$$TUF = \frac{2\sqrt{2}}{\pi^2} \frac{RL}{R_f + RL} = \frac{2\sqrt{2}}{\pi^2} \frac{1}{\left(\frac{R_f + RL}{RL}\right)}$$

$$TUF = \frac{2\sqrt{2}}{\pi^2} \frac{1}{\left(\frac{R_f}{RL} + 1\right)}$$

if  $R_L \gg R_f$

$$TUF = \frac{2\sqrt{2}}{\pi^2}$$

$$TUF = 0.287 //$$

$$\therefore TUF = 28.7 \% //$$

(7) Form factor (FF):

~~~~ ~~~~ ~~~~ ~~~~

$$FF = \frac{\text{rms value}}{\text{average value}} = \frac{I_m/2}{I_m/\pi} = 1.5 \cancel{f//}$$

(8) Peak factor (PF):

~~~~ ~~~~ ~~~~

$$PF = \frac{\text{peak value}}{\text{Rms value}} = \frac{I_m}{I_m/2} = 2 \cancel{/}$$

(9)

## Centre-tap full wave Rectifier:

(i) DC component & Average current ( $I_{dc}$ ):

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i d\theta$$

$$\left[ \begin{array}{l} \cos \pi = -1 \\ \cos 2\pi = 1 \\ \cos 0 = 1 \end{array} \right]$$

$$\begin{aligned} I_{dc} &= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \theta d\theta + \frac{1}{2\pi} \int_{\pi}^{2\pi} -I_m \sin \theta d\theta \\ &= \frac{1}{2\pi} \left[ I_m (-\cos \theta) \Big|_0^{\pi} - I_m (-\cos \theta) \Big|_{\pi}^{2\pi} \right] \\ &= -\frac{I_m}{2\pi} [(-1 - 1) - (1 + 1)] = \frac{2I_m}{2\pi} \end{aligned}$$

$$I_m = \frac{V_m}{(R_f + R_L)}$$

$$I_{dc} = \frac{2I_m}{\pi} \quad \text{--- (1)}$$

Similarly

$$I_{dc} = \frac{2V_m}{\pi(R_f + R_L)}$$

$$V_{dc} = \frac{2V_m}{\pi} \quad \text{--- (2)}$$

(ii) Root mean square current ( $I_{rms}$ ):

$$\begin{aligned} I_{rms} &= \frac{1}{2\pi} \int_0^{2\pi} I^2 d\theta \\ &= \frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \theta d\theta \\ &= \frac{I_m^2}{2\pi} \int_0^{2\pi} \left[ \frac{1 - \cos 2\theta}{2} \right] d\theta \\ &= \frac{I_m^2}{4\pi} \left[ (\theta) \Big|_0^{2\pi} - \left( \frac{\sin 2\theta}{2} \right) \Big|_0^{2\pi} \right] \end{aligned}$$

$$\frac{Im^2}{4\pi} [(2\pi - \delta) - (0 - \delta)] = \frac{Im^2}{2}$$

$$\therefore I_{rms} = \frac{Im}{\sqrt{2}} \quad \text{--- (3)}$$

(iii) Voltage Regulation :

→ The variation of dc % voltage as a function of d.c. load current is called Regulation.

$$\% \text{ Regulation} = \frac{V_{no\text{load}} - V_{Full\text{load}}}{V_{full\text{load}}} \times 100\% \quad \text{--- (4)}$$

$$\% \text{ Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \quad \text{--- (5)}$$

$$V_{NL} = \frac{2Vm}{\pi} \quad \text{--- (6)}$$

$$V_{FL} = \frac{2Vm}{\pi} - I_{dc} R_f \quad \text{--- (7)}$$

$$V_{FL} = \frac{2Vm}{\pi} - \frac{2Vm}{\pi} \frac{R_f}{R_f + R_L} \quad \left[ \because I_{dc} = \frac{2Vm}{\pi(R_f + R_L)} \right]$$

$$V_{FL} = \frac{2Vm}{\pi} \left[ 1 - \frac{R_f}{R_f + R_L} \right]$$

$$V_{FL} = \frac{2Vm}{\pi} \left[ \frac{R_f + R_L - R_f}{R_f + R_L} \right]$$

$$V_{FL} = \frac{2Vm}{\pi} \frac{R_L}{R_f + R_L} \quad \text{--- (8)}$$

$e_V(5)$  &  $e_V(7)$  in  $e_V(4)$

(11)

$$\% \text{ Regulation} = \frac{\frac{2V_m}{\pi} - \frac{2V_m}{\pi} \frac{R_L}{R_f + R_L}}{\frac{2V_m}{\pi} \frac{R_L}{R_f + R_L}}$$

$$= \frac{\cancel{\frac{2V_m}{\pi}} \left[ 1 - \frac{R_L}{R_f + R_L} \right]}{\cancel{\frac{2V_m}{\pi}} \frac{R_L}{R_f + R_L}}$$

$$= \frac{\left[ \frac{R_f + R_L - R_L}{R_f + R_L} \right]}{\frac{R_L}{R_f + R_L}}$$

$\% \text{ Regulation} = \frac{R_f}{R_L} \times 100$

→ ⑧

(iv) Ripple factor:

$$r = \frac{\text{rms value of a.c. Components of o/p wave}}{\text{dc value of the o/p wave}}$$

$$r = \frac{I_{ac}}{I_{dc}} \quad \text{--- ⑨.}$$

effective value of the pulsating o/p current

$$I_{rms} = I_{ac} + I_{dc}$$

$$I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

(12)

$$r = \sqrt{\frac{I_{rms} - I_{dc}}{I_{dc}}}$$

$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - \frac{I_{dc}^2}{I_{dc}^2}}$$

$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} \quad \rightarrow (10)$$

$$\begin{aligned} \therefore I_{dc} &= \frac{2Im}{\pi} \\ \therefore I_{rms} &= \frac{Im}{\sqrt{2}} \end{aligned}$$

$$r = \sqrt{\left(\frac{\frac{Im}{\sqrt{2}}}{\frac{2Im}{\pi}}\right)^2 - 1}$$

$$r = \sqrt{\frac{\frac{I_{dc}^2}{2} \times \frac{\pi^2}{4Im}}{I_{dc}^2}} - 1$$

$$r = \sqrt{\frac{\pi^2}{8} - 1} = 0.482$$

$$r = 0.482$$

## V) Efficiency of Fullwave Rectifier:

(13)

The ratio of d.c. o/p power to a.c. i/p power

$$\eta = \frac{\text{d.c. o/p power}}{\text{a.c. i/p power}}$$

$$\eta = \frac{P_{dc}}{P_{ac}} \quad \text{--- (11)}$$

$$P_{dc} = \frac{\tilde{V}_{dc}}{R_L} \quad \text{--- (12)}$$

$$P_{ac} = \frac{\tilde{V}_{rms}}{R_L} \quad \text{--- (13)}$$

$\eta$  (12) &  $\eta$  (13) in eq (11)

$$\eta = \frac{\tilde{V}_{dc}/R_L}{\tilde{V}_{rms}/R_L}$$

$$\eta = \frac{\tilde{V}_{dc}}{\tilde{V}_{rms}}$$

$$\left[ \begin{array}{l} \because \tilde{V}_{dc} = \frac{2Vm}{\pi} \\ \therefore \tilde{V}_{rms} = \frac{Vm}{\sqrt{2}} \end{array} \right]$$

$$\eta = \frac{\left(\frac{2Vm}{\pi}\right)^2}{\left(\frac{Vm}{\sqrt{2}}\right)^2} = \frac{4Vm^2}{\pi^2} \times \frac{2}{Vm^2}$$

$$\eta = \frac{8}{\pi^2} = 0.812$$

$$\boxed{\eta \cdot \eta = 81.2\%}$$

→ Transformer utilization factor (TUF) in full wave Rectifier:

→ A FWR has '2' windings across the Transformer secondary

$$\text{therefore, } TUF_{\text{secondary}} = 2 \times TUF_{\text{primary}}$$

$$= 2 \times 0.287 = 0.574$$

→ TUF primary is defined as the ratio of dc op delivered to the load to the ac rating of the transformer primary.

$$TUF = \frac{P_{dc}}{P_{ac(\text{rated})}} = \frac{I_{dc} R_L}{I_{rms} \times V_{rms} (\text{rated})}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}, \quad I_{dc} = \frac{2I_m}{\pi}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{I_m (R_f + R_L)}{\sqrt{2}} = \frac{I_m R_L}{\sqrt{2}}$$

$$\begin{aligned} TUF &= \frac{\left(\frac{2I_m}{\pi}\right) R_L}{\frac{I_m}{\sqrt{2}} \times \frac{I_m R_L}{\sqrt{2}}} = \frac{\frac{4I_m^2}{\pi^2} R_L}{\frac{I_m^2 R_L}{2}} \\ &= \frac{\frac{4I_m^2 R_L}{\pi^2} \times 2}{\frac{I_m^2 R_L}{2}} = \frac{8}{\pi^2} = 0.812 \end{aligned}$$

$$\text{Therefore average TUF} = \frac{0.574 + 0.812}{2} = 0.693$$

→ form factor :

$$\text{form factor} = \frac{\text{sms value of the o/p voltage}}{\text{average value of the o/p voltage}}$$

$$= \frac{V_m/\sqrt{2}}{2V_m/\pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

~~1.11~~

→ peak factor :

$$\text{peak factor} = \frac{\text{peak value of the o/p voltage}}{\text{sms value of the o/p voltage}}$$

$$= \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2}$$

~~$\sqrt{2}$~~

→ Comparison b/w half wave, center tap & bridge Rectifiers: (16)

| Characteristics             | Half wave<br>Rectifiers                | Full wave Rectifiers                     |                         |
|-----------------------------|--|--|-------------------------|
|                             |  | Center tap                               | Bridge                  |
| No. of Diodes               | 1                                      | 2  | 4                       |
| Transformer requirement     | Not <del>so</del> essential            | essential                                | not essential           |
| $I_{dc}$                    | $\frac{I_m}{\pi}$                      | $\frac{2I_m}{\pi}$                       | $\frac{2I_m}{\pi}$      |
| $I_{rms}$                   | $\frac{I_m}{\sqrt{2}}$                 | $\frac{I_m}{\sqrt{2}}$                   | $\frac{V_m}{RL + 2R_f}$ |
| $I_m$                       | $\frac{V_m}{R_f + RL}$                 | $\frac{V_m}{R_f + RL}$                   | $\frac{2I_m RL}{\pi}$   |
| $V_{dc}$                    | $\frac{I_m RL}{\pi} = \frac{V_m}{\pi}$ | $\frac{2I_m RL}{\pi} = \frac{2V_m}{\pi}$ | $\frac{2I_m RL}{\pi}$   |
| $\eta$                      | 40.6%                                  | 81.2%                                    | 81.2%                   |
| TUF                         | 0.286                                  | 0.693                                    | 0.812                   |
| fundamental freq. of ripple | f                                      | 2f                                       | 2f                      |
| Ripple factor (r)           | 1.21                                   | 0.482                                    | 0.482                   |
| voltage regulation          | Good                                   | Better                                   | Good                    |